

Security Door lock System



Problem Statement & Objective

The Challenge: For Goddard, injury, or physically impaired individuals, getting out of bed to physically unlock a door for family members or medical staff, is an impossible task.

My Solution: A custom library prototype built on the Arduino **UNO** that lets a patient safely open their door directly from their pillow using a wireless remote, while offering a complete local backup via SD card.



Core Hardware Architecture

*Therapsites* for *unatidina*

System Execution Logic

Problem Statement & Objective

The Challenge: For bedridden, elderly, or physically impaired individuals, getting out of bed to physically unlock a door for family members or medical staff causes immense strain.

My Solution: A budget friendly prototype built on the **Arduino UNO** that lets a patient safely open their door directly from their pillow using a wireless remote, while allowing caregivers local tap access via RFID.



Core Hardware Architecture


- Arduino UNO R3
- 433MHz RF Transmitter & Receiver pair (Bypasses walls and obstacles).
- MFRC522 RFID Kit (Proximity badge scanning at the door).
- 16x2 LCD Module with I2C backpack.
- Red & Green LEDs paired with a 5V Active Buzzer for instant sensory feedback.

Transmitter

Receiver



Detailed Circuit Architecture

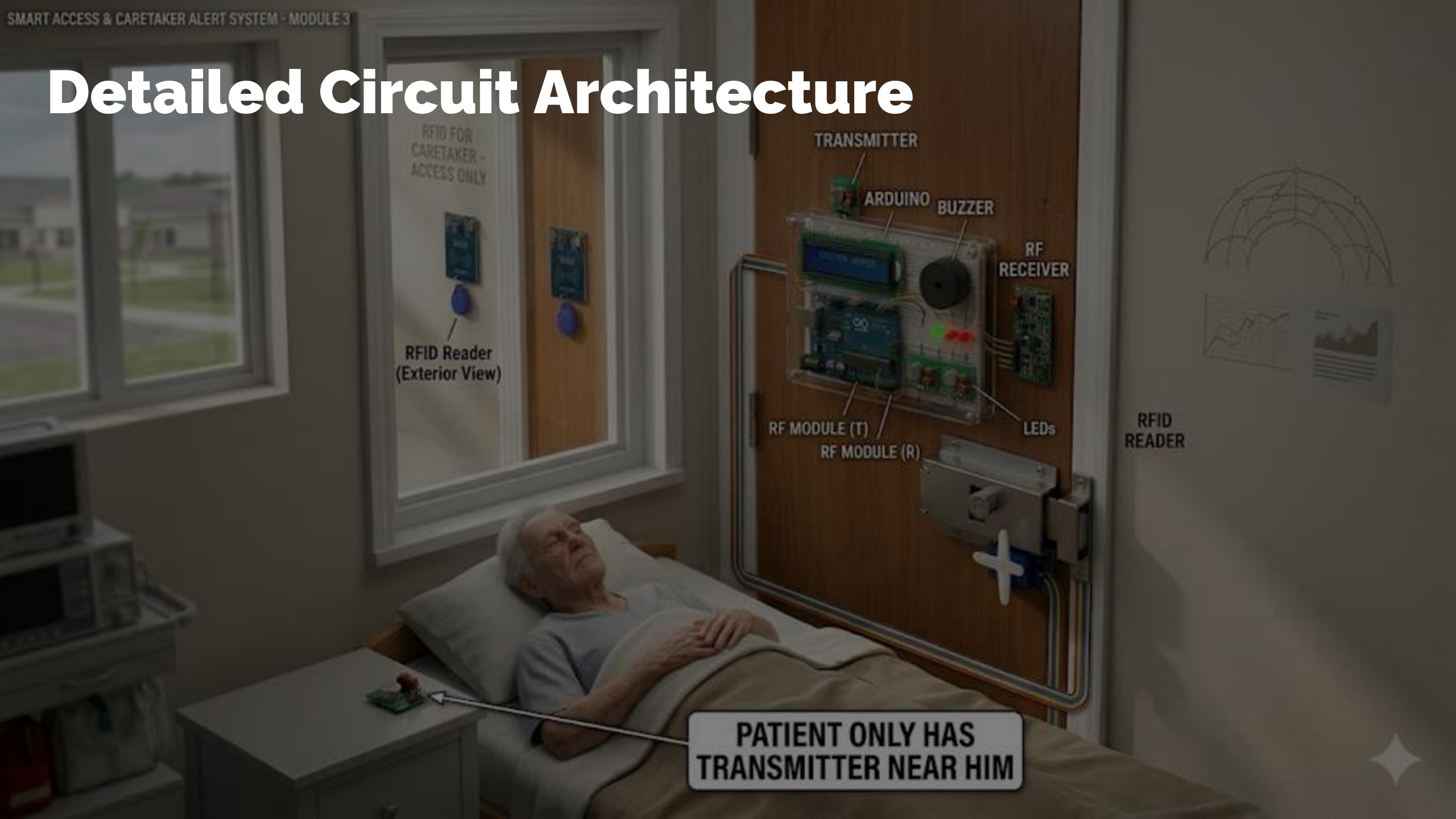

RFID Reader
(Exterior View)

TRANSMITTER

ARDUINO

BUZZER

RF
RECEIVER

RF MODULE (T)

RF MODULE (R)

LEDs

RFID
READER

PATIENT ONLY HAS
TRANSMITTER NEAR HIM

Component Category	Component	Pin Label	Connect To (Arduino/Breadboard)	Notes
Logic & Data	I2C LCD 16x2	GND	Breadboard GND (-)	Common Ground
		VCC	Breadboard 5V (+)	
		SDA	Analog Pin A4	I2C Data Line
		SCL	Analog Pin A5	I2C Clock Line
Authentication	MFRC522 RFID Reader	VCC	Arduino 3.3V Pin	Warning: 3.3V ONLY!
		RST	Digital Pin D9	Reset
		GND	Breadboard GND (-)	Common Ground
		MISO	Digital Pin D12	SPI Pin
		MOSI	Digital Pin D11	SPI Pin
		SCK	Digital Pin D13	SPI Pin
		SDA (SS)	Digital Pin D10	Slave Select
Long Range	433MHz RF Receiver	VCC	Breadboard 5V (+)	
		DATA	Digital Pin D2	MUST be D2 (Interrupt 0)
		GND	Breadboard GND (-)	Common Ground
Indicators	Green LED (D3)	Long Leg	Digital Pin D3	
	Red LED (D4)	Long Leg	Digital Pin D4	
	Active Buzzer (5V)	Positive Leg	Digital Pin D5	Short leg to GND
Mechanical Actuation	SG90 Micro Servo Motor	Brown Wire	Breadboard GND (-)	Ground
		Red Wire	Arduino 5V Pin	Power
		Orange Wire	Digital Pin D6	Servo PWM Signal

System Execution Logic

Patient-Initiated Access: The patient uses a handheld **433MHz RF remote** from their bedside. Because the system utilizes radio frequency (RF) signals, the command penetrates walls and obstacles, allowing the user to unlock the door without physical effort.

Caregiver Access: Visiting medical staff or family use an **RFID key fob**, which they simply tap against an external reader to gain entry.

The Arduino validates both inputs against pre stored secure data:

Access Granted: The system confirms a match, updates the **LCD display**, illuminates the **Green LED**, sounds a confirming **double beep**, and triggers a **servo operated latch** to unlock the door for 5 seconds before automatically relocking.

Access Denied: If an unauthorized token is detected, the system immediately rejects entry by flashing the **Red LED**, sounding a **continuous alarm buzzer**, and displaying an "Invalid Token" error on the LCD.

Future Scope & Mechanical Completion



- High-Torque Actuation (MG996R)
- **Deadbolt Latch System**
- Transitioning to an ESP32 architecture to enable real-time entry timestamp

Thanks for watching

Muhammad Haseeb Ul Hassan 281131349